

**Solutions to Problems Marked with a * in
Logic and Computer Design Fundamentals, 3rd Edition**

Chapter 10

(Updated 9/21/06) © 2004 Pearson Education, Inc.

10-2.*

$$C = C_8$$

$$V = C_8 \oplus C_7$$


$$Z = \overline{F_7} + F_6 + F_5 + F_4 + F_3 + F_2 + F_1 + F_0$$

$$N = F_7$$

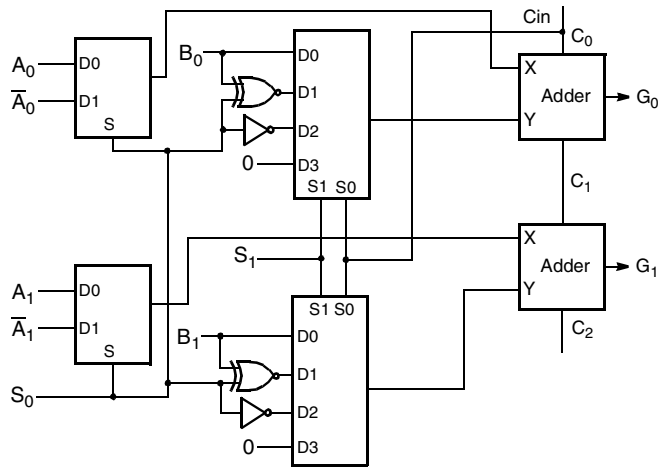
10-3.*

$$X = S_0 \overline{A} + \overline{S_0} A$$

$$Y = \overline{S_1} \overline{C_{in}} B + \overline{S_1} S_0 B + \overline{S_1} \overline{S_0} \overline{B} + S_1 \overline{S_0} \overline{C_{in}}$$



10-4.*

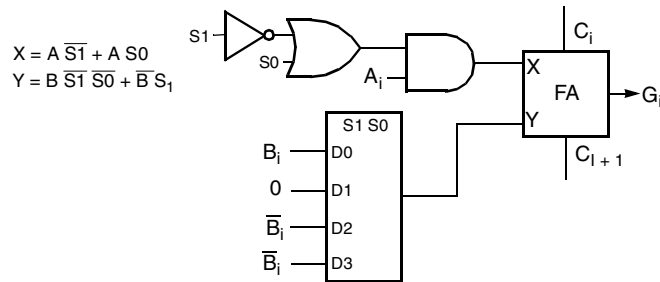

$$X = A \overline{S_1} + A S_0$$

$$Y = B \overline{S_1} \overline{S_0} + \overline{B} S_1$$

10-6.*(Updated 9/21/06)

- a) XOR = 00, NAND = 01, NOR = 10 XNOR = 11
 Out = $S_1 \overline{A} \overline{B} + \overline{S_1} A \overline{B} + \overline{S_1} \overline{A} B + S_1 S_0 A B$ + (one of $S_0 \overline{A} \overline{B}$ or $\overline{S_1} S_0 \overline{A}$)
- b) The above is a simplest result.

10-8.*

- (a) 0101 (b) 0110 (c) 1010 (d) 0110

10-10.*

Problem Solutions – Chapter 10

- | | | | | | |
|-----|-----------------------------------------|----------------|-----|----------------------------|----------------|
| (a) | $R5 \leftarrow R4 \wedge \overline{R5}$ | R5 = 0000 0100 | (d) | $R5 \leftarrow R0$ | R5 = 0000 0000 |
| (b) | $R6 \leftarrow R2 + \overline{R4} + 1$ | R6 = 1111 1110 | (e) | $R4 \leftarrow srConstant$ | R4 = 0000 0011 |
| (c) | $R5 \leftarrow R0$ | R5 = 0000 0000 | (f) | $R3 \leftarrow Data\ in$ | R3 = 0001 1011 |

10-14.*

- a) Opcode = 7 bits b) 20 bits c) 1,048,576 d) -524288 to +524287