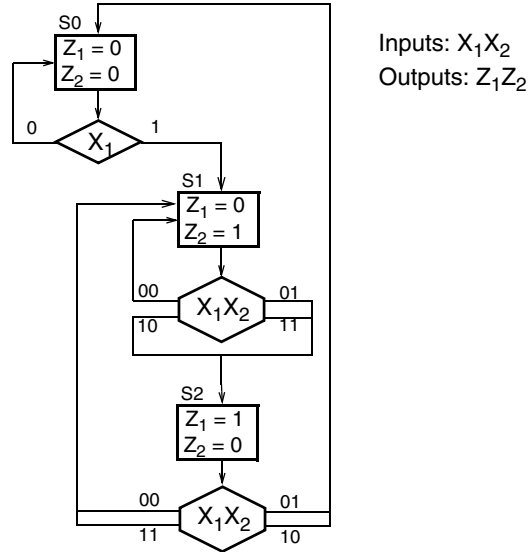


Solutions to Problems Marked with a * in
Logic and Computer Design Fundamentals, 3rd Edition

Chapter 8

(Updated 9/21/06) © 2004 Pearson Education, Inc.


8-1.*(Updated 9/21/06)



8-2.*

A:	0	1	1	0	1	1	0	1	
B:	1	1	0	1	0	1	0	1	
C:	0	1	0	1	0	1	0	1	
State:	ST1	ST1	ST2	ST3	ST1	ST2	ST3	ST1	ST2
Z:	0	0	0	1	0	1	1	0	0

8-5.*

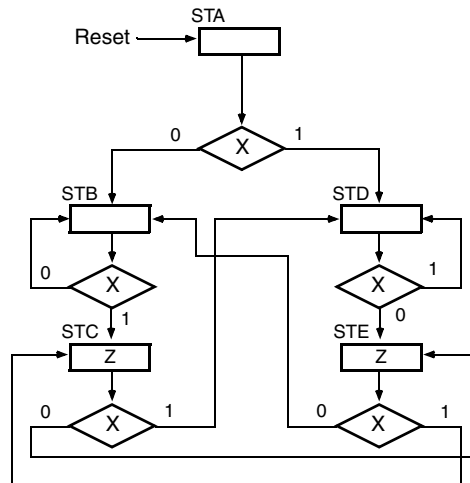

8-8.*


$ST1(t+1) = ST1 \cdot \bar{A} + ST2 \cdot B \cdot \bar{C} + ST3$, $ST2(t+1) = ST1 \cdot A$, $ST3(t+1) = ST2 \cdot (\bar{B} + C)$, $Z = ST2 \cdot B + ST3$
 For the D flip-flops, $D_{STi} = STi(t+1)$ and $STi = Q_{STi}$. Reset initializes the flip-flops: $ST1 = 1$, $ST2 = ST3 = 0$.

Problem Solutions – Chapter 8

8-9.*

State Assignment

	Y1	Y0
ST1	0	0
ST2	0	1
ST3	1	0

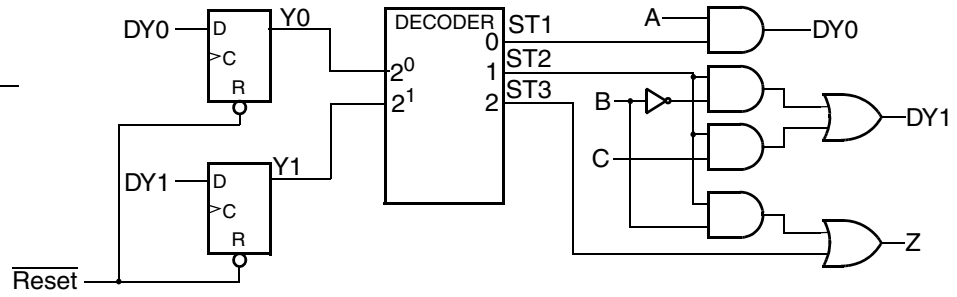

8-11.*


```

100110 (38)
× 110101 (× 53)
-----
100110
000000
100110
000000
100110
100110
11111011110 (2014)
    
```


```


100110
110101
-----
000000      Init PP
100110      Add
100110      After Add
0100110     After Shift
00100110   After Shift
100110      Add
10111110   After Add
01011110   After Shift
001011110  After Shift
100110      Add
110001110  After Add
0110001110 After Shift
100110      Add
1111101110 After Add
0111101110 After Shift
    
```

8-16.*

 

 R is a synchronous reset that overrides any simultaneous synchronous transfer.



 

8-19.*

```

library IEEE;
use IEEE.std_logic_1164.all;

entity asm_819 is
    port (
        A, B, C, CLK, RESET: in STD_LOGIC;
        Z: out STD_LOGIC
    );
end asm_819;

architecture asm_819_arch of asm_819 is
    type state_type is (ST1, ST2, ST3);
    signal state, next_state : state_type;
begin


    state_register: process (CLK, RESET)
    begin
        if RESET='1' then--asynchronous RESET active High
            state <= ST1;
        elsif (CLK'event and CLK='1') then --CLK rising edge
            state <= next_state;
        end if;
    end process;

    next_state_func: process (A, B, C, state)
    begin
        case (state) is
            when ST1 =>
                if A = '0' then
                    next_state <= ST1;
                else
                    next_state <= ST2;
                end if;
            when ST2 =>
                if ((B = '1') and (C = '0')) then
                    next_state <= ST1;
                else
                    next_state <= ST3;
                end if;
            when ST3 =>
                next_state <= ST1;
        end case;
    end process;

    output_func: process (B, state)
    begin
        case (state) is
            when ST1 =>
                Z <= '0';
            when ST2 =>
                if (B = '1') then
                    Z <= '1';
                else
                    Z <= '0';
                end if;
            when ST3 =>
                Z <= '1';
        end case;
    end process;
end asm_819_arch;

```

Problem Solutions – Chapter 8

 

8-20.*

```

module asm_820 (CLK, RESET, A, B, C, Z);
input CLK, RESET, A, B, C;
output Z;
reg [1:0] state, next_state;
parameter ST1=2'b00, ST2=2'b01, ST3=2'b10;
reg Z;

//State register
always @(posedge CLK or posedge RESET)
begin
if (RESET) //asynchronous RESET active High
state <= ST1;
else //use CLK rising edge
state <= next_state;
end

//Next state function
always @(A or B or C or state)
begin
case (state)
ST1: next_state <= A ? ST2: ST1;
ST2: next_state <= (B && !C) ? ST1: ST3;
ST3: next_state <= ST1;
default: next_state <= ST1;
endcase
end

//Output function
always @(B or state)
begin
case (state)
ST1: Z <= 1'b0;
ST2: Z <= B ? 1'b1: 1'b0;
ST3: Z <= 1'b1;
default: Z <= 0'b0;
endcase
end
endmodule

```

